

# Transitivity

$$\begin{array}{l}
 p \rightarrow q \\
 q \rightarrow r \\
 \hline
 \therefore p \rightarrow r
 \end{array}$$

| p | q | r | $p \rightarrow q$ | $q \rightarrow r$ | $p \rightarrow r$ |
|---|---|---|-------------------|-------------------|-------------------|
| T | T | T | T                 | T                 | T                 |
| T | T | F | F                 | F                 | F                 |
| T | F | T | T                 | T                 | T                 |
| T | F | F | T                 | T                 | T                 |
| F | T | T | T                 | T                 | T                 |
| F | T | F | T                 | F                 | F                 |
| F | F | T | T                 | T                 | T                 |
| F | F | F | T                 | T                 | T                 |

Division into cases

$$\begin{array}{l} p \vee q \\ p \rightarrow r \\ \hline q \rightarrow r \\ \dots \\ \dots \end{array}$$

$$\begin{array}{l} P \rightarrow q \\ P \\ \hline \therefore q \\ \text{valid} \end{array}$$
$$\begin{array}{l} P \rightarrow q \\ q \\ \hline \therefore P \\ \text{invalid} \end{array}$$

contradiction rule


$$\neg p \rightarrow c$$
$$\therefore P$$

| $p$ | $\neg p$ | $c$ | $\neg p \rightarrow c$ | $i$ |
|-----|----------|-----|------------------------|-----|
| T   | F        | F   | T                      | ←   |
| F   | T        | F   | F                      |     |


# Digital logic circuits

## Gates

and

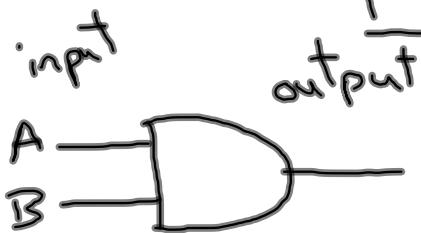

or

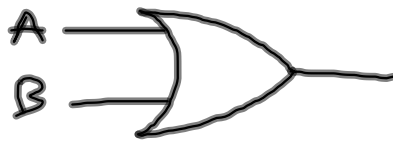


not





| A | B | A and B |
|---|---|---------|
| 1 | 1 | 1       |
| 1 | 0 | 0       |
| 0 | 1 | 0       |
| 0 | 0 | 0       |



$$p \vee \sim q$$

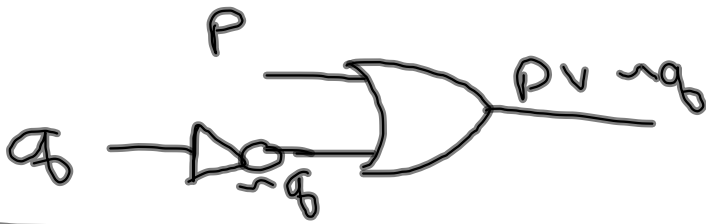

---
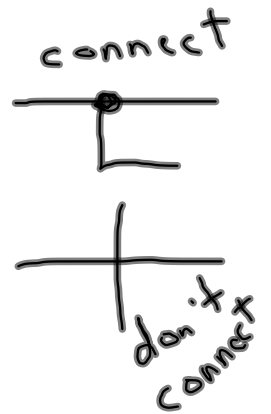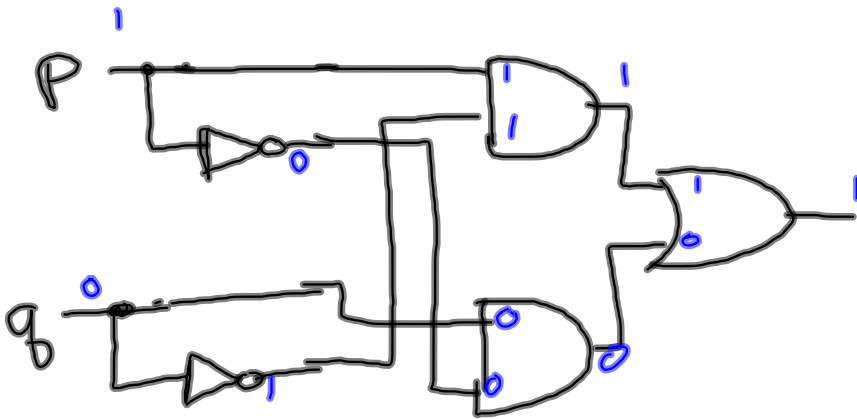
$$(p \wedge \sim q) \vee (q \wedge \sim p)$$



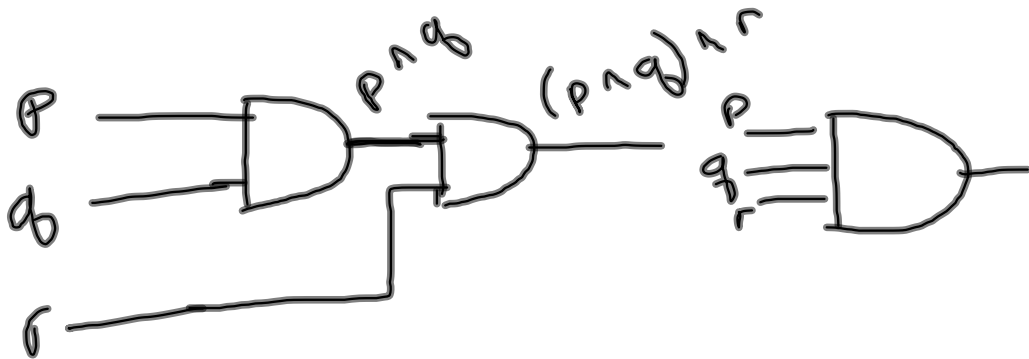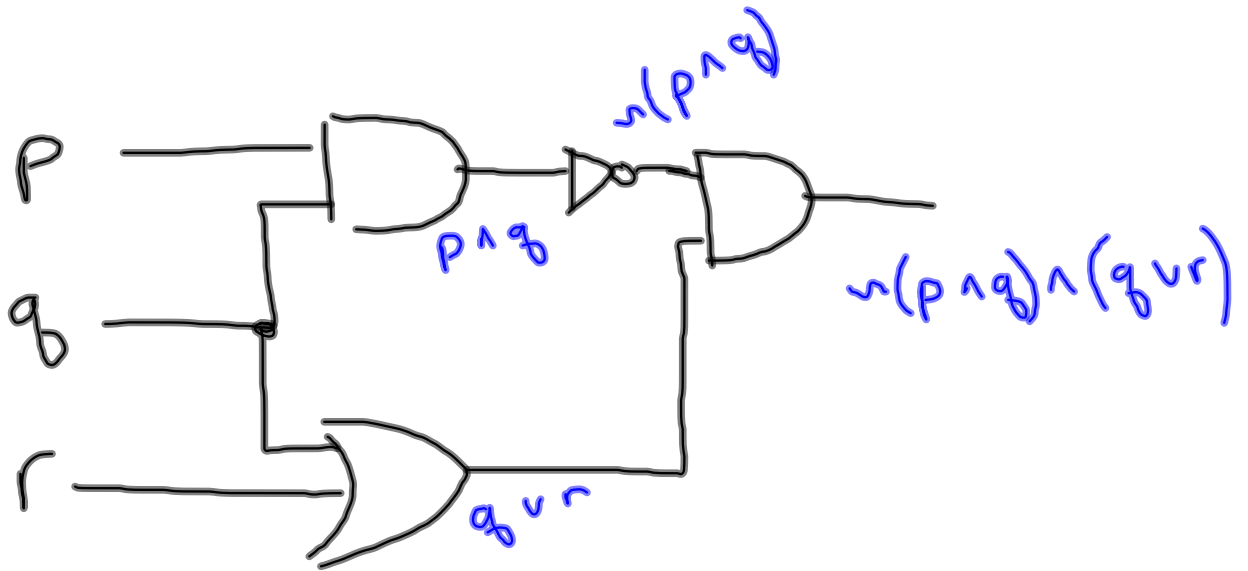


| p | q | r | F | a | b | c | d |
|---|---|---|---|---|---|---|---|
| - | - | - | - | ↑ | 1 | 0 | 0 |
| - | 0 | 0 | - | ↑ | 0 | 1 | 0 |
| 0 | - | 0 | - | ↑ | 0 | 0 | 1 |
| 0 | 0 | - | - | ↑ | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 |   | 0 | 0 | 0 |

$a = p \wedge q \wedge r$   
 $b = p \wedge \neg q \wedge r$   
 $c = \neg p \wedge q \wedge r$   
 $d = \neg p \wedge q \wedge \neg r$

$F = a \vee b \vee c \vee d$

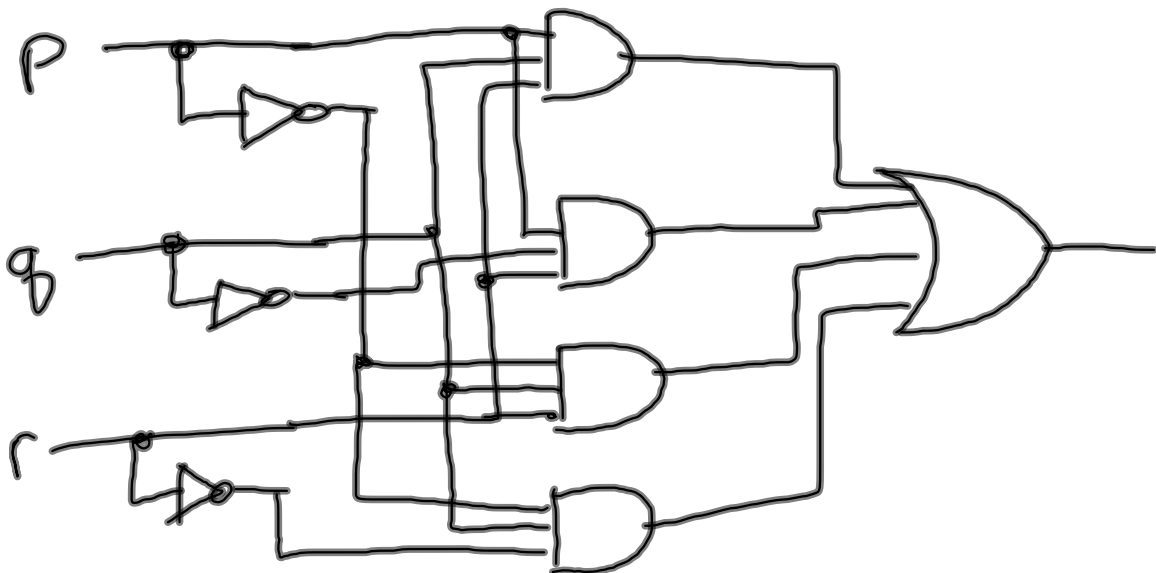$F = (p \wedge q \wedge r) \vee (p \wedge \neg q \wedge r) \vee (\neg p \wedge q \wedge r) \vee (\neg p \wedge q \wedge \neg r)$





and, or and not - can be used to produce any Boolean formula. (computationally complete)

NAND - (not and)

computationally complete

| p | q | p nand q |
|---|---|----------|
| 1 | 1 | 0        |
| 1 | 0 | 1        |
| 0 | 1 | 1        |
| 0 | 0 | 1        |



Not (w/ nand)

$$\sim(p \wedge p) \equiv \sim p$$

