

AND: AB

OR: $A+B$

Not: \bar{A}

A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A}\bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$$\overline{(A+B)} \equiv \bar{A}\bar{B}$$

also

$$\overline{AB} \equiv \bar{A} + \bar{B}$$

DeMorgan's
Law

$$\overline{A} \overline{B} \neq \overline{AB}$$

A	B	$\overline{A} \overline{B}$	AB	\overline{AB}
0	0	1	0	1
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0

A	B	C	BC	A	A+BC	(1) A+B	(2) A+C	(1)(2)
0	0	0	0		0	0	0	0
0	0	1	0		0	0	0	0
0	1	0	0		0	1	0	0
0	1	1	1		1	1	1	1
1	0	0	0		1	1	1	1
1	0	1	0		1	1	1	1
1	1	0	0		1	0	1	0
1	1	1	1		1	0	1	0

$$A + BC \equiv (A+B)(A+C)$$

A	B	F	f_1	f_2
0	0	1	1	0
0	1	0	0	0
1	0	1	0	1
1	1	0	0	0



$$F = f_1 + f_2$$

$$f_1 = \bar{A}\bar{B} \quad f_2 = A\bar{B}$$

$$F = \bar{A}\bar{B} + A\bar{B}$$


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
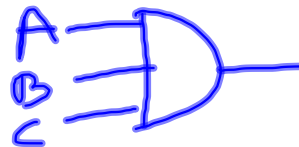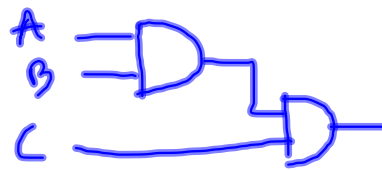
$$F = \bar{A}BC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$




Gates


AND

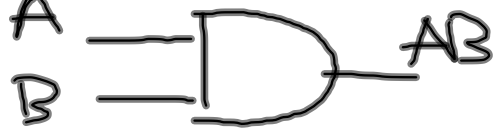

OR

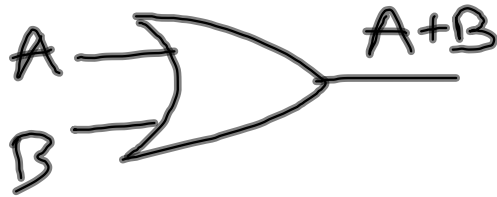

NOT

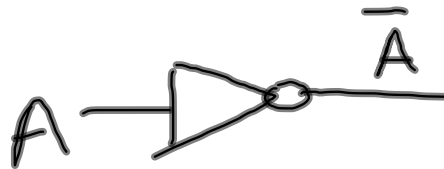


logisim

AND/OR/NOT

computationally complete
set of operators

NAND gate

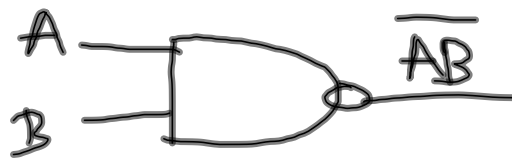

create
AND, OR, NOT

NOT :

A \bar{A}

$$AA \equiv A$$

$$\bar{A}\bar{A} \equiv \bar{A}$$

AND :

$$AB \equiv \overline{\overline{AB}}$$

← NOT
NAND

$$\overline{AB} \equiv \bar{A} + \bar{B}$$

OR :

$$A + B \equiv \overline{\bar{A}\bar{B}}$$

$$\overline{A+B} \equiv \bar{A}\bar{B}$$